

Digital Logic Design + Computer Architecture

Sayandeep Saha

Assistant Professor
Department of Computer
Science and Engineering
Indian Institute of Technology
Bombay



CPU Datapath

What is “Datapath” for a Processor?

- Same as the datapath control split we studied for GCD processor.
 - **Datapath processes the data**
 - **Controller tells how to process the data**
- But here it’s for processing the instructions in an ISA
- A datapath that can process all the instructions in an ISA



Image generated by ChatGPT

Datapath Elements

- We shall begin with the simplest case
 - Every instruction finishes in **one clock cycle**
 - The clock frequency is determined by the instruction finishes last
- Remember, again how we constructed the GCD datapath
- Let's first identify what are the components needed

 


Image generated by ChatGPT


Datapath Elements

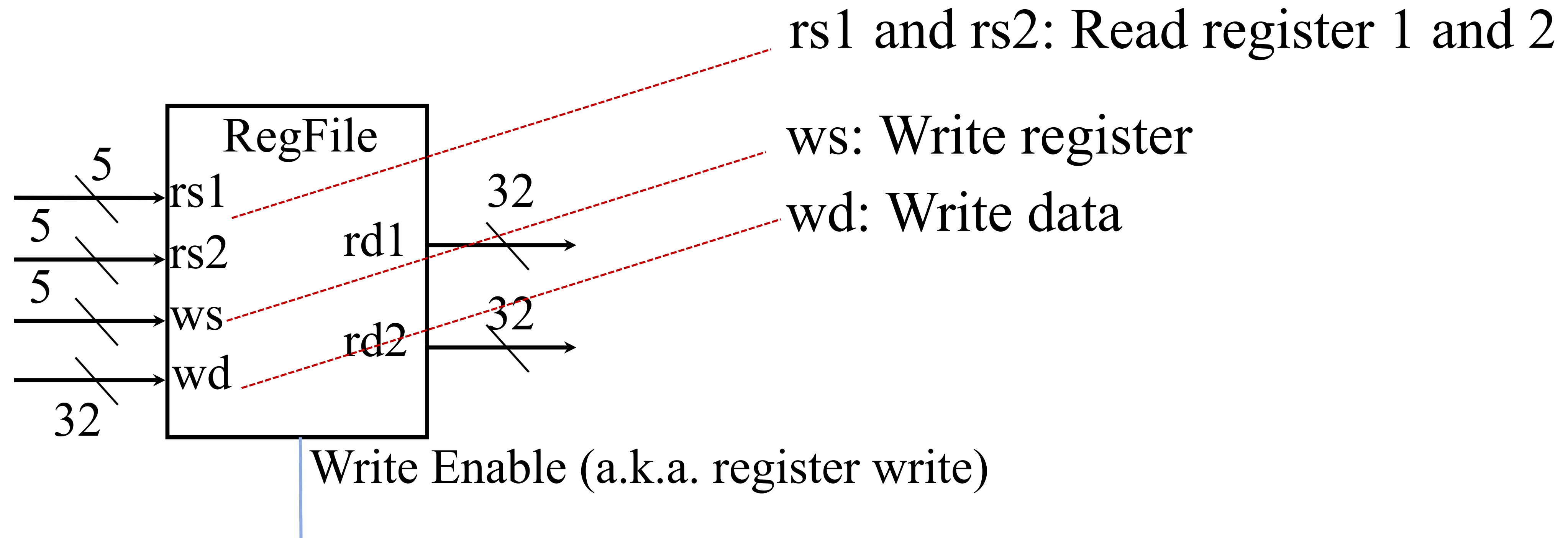- Remember, again how we constructed the GCD datapath
- Let's first identify what are the components needed

 


Image generated by ChatGPT

Datapath Elements: Register File




Datapath Elements: The ALU




- All arithmetic and logical operation happens here
- Operation selection
- E.g.,
 - $Op = 0: Y = A + B$
 - $Op = 1: Y = A - B$
 - $Op = 2; Y = A * B$

Datapath Elements: Program Counter

 - Remember PC register??
- It always points to the next instruction to be executed...
- But where is the next instruction???




Datapath Elements: Instruction Memory

 

Remember: No writes to instruction memory

Not concerned about how programs are loaded into this memory.


Datapath Elements: Data Memory

 

Why data and instruction memory and not one memory?

- Recall Harvard vs. Von Neuman
- Not so simple matter, will discuss later.

Datapath Elements: Data Memory

 

Why data and instruction memory and not one memory?

- Recall Harvard vs. Von Neuman
- Not so simple matter, will discuss later.

Datapath Elements: Buses

- Same as your public transport
- Transfer data and instructions
- Separate buses for address and data




Datapath Elements: Buses

- Same as your public transport
- Transfer data and instructions
- Separate buses for address and data
 - Why???




Datapath Elements: Timing Diagram

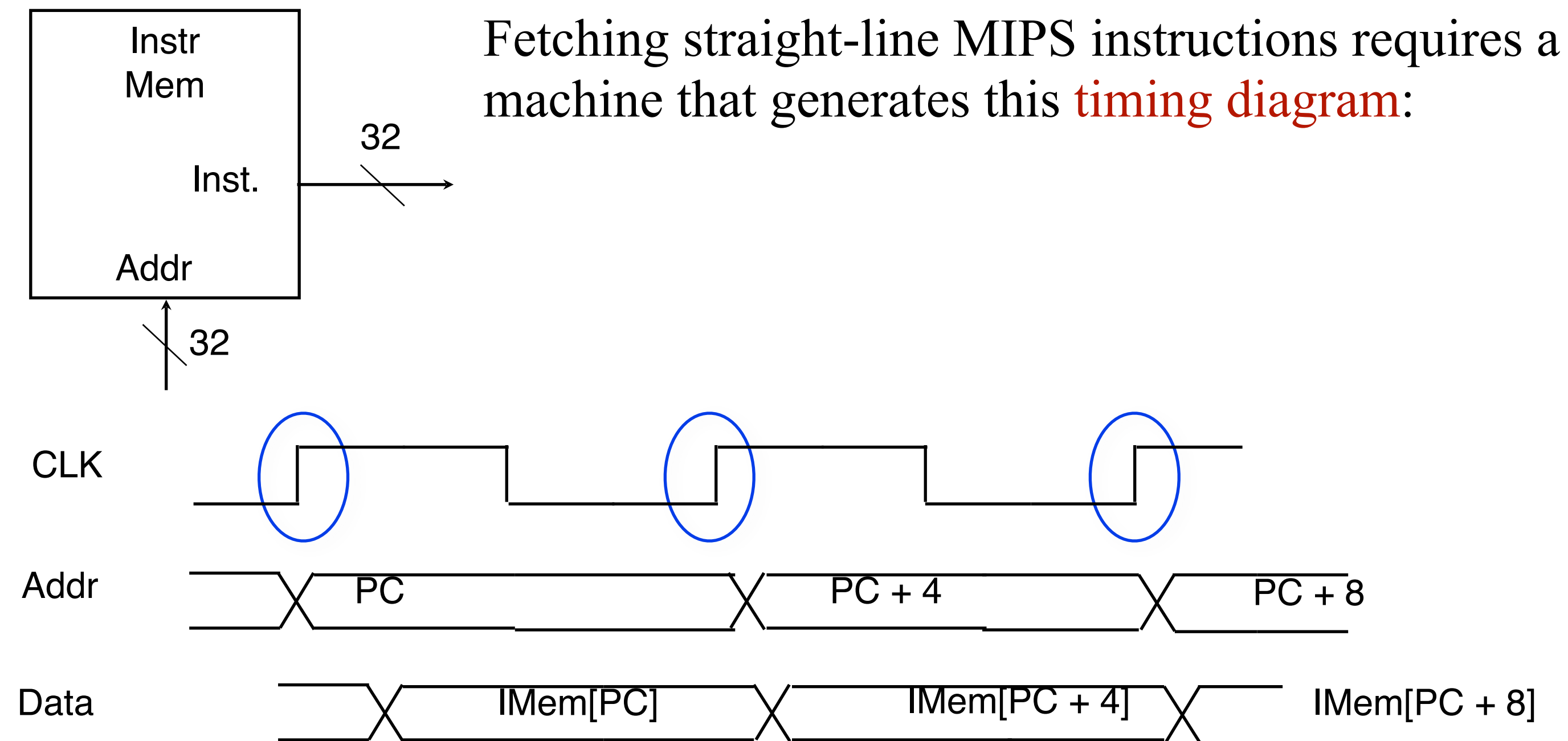


- Every clock cycle we process one instruction (super simple)
- Sending the PC and getting the instruction from memory is called **Instruction Fetch**

PC == Program Counter, points to next instruction.


Datapath Elements: Decoding Instructions

 


Datapath Elements: Decoding Instructions

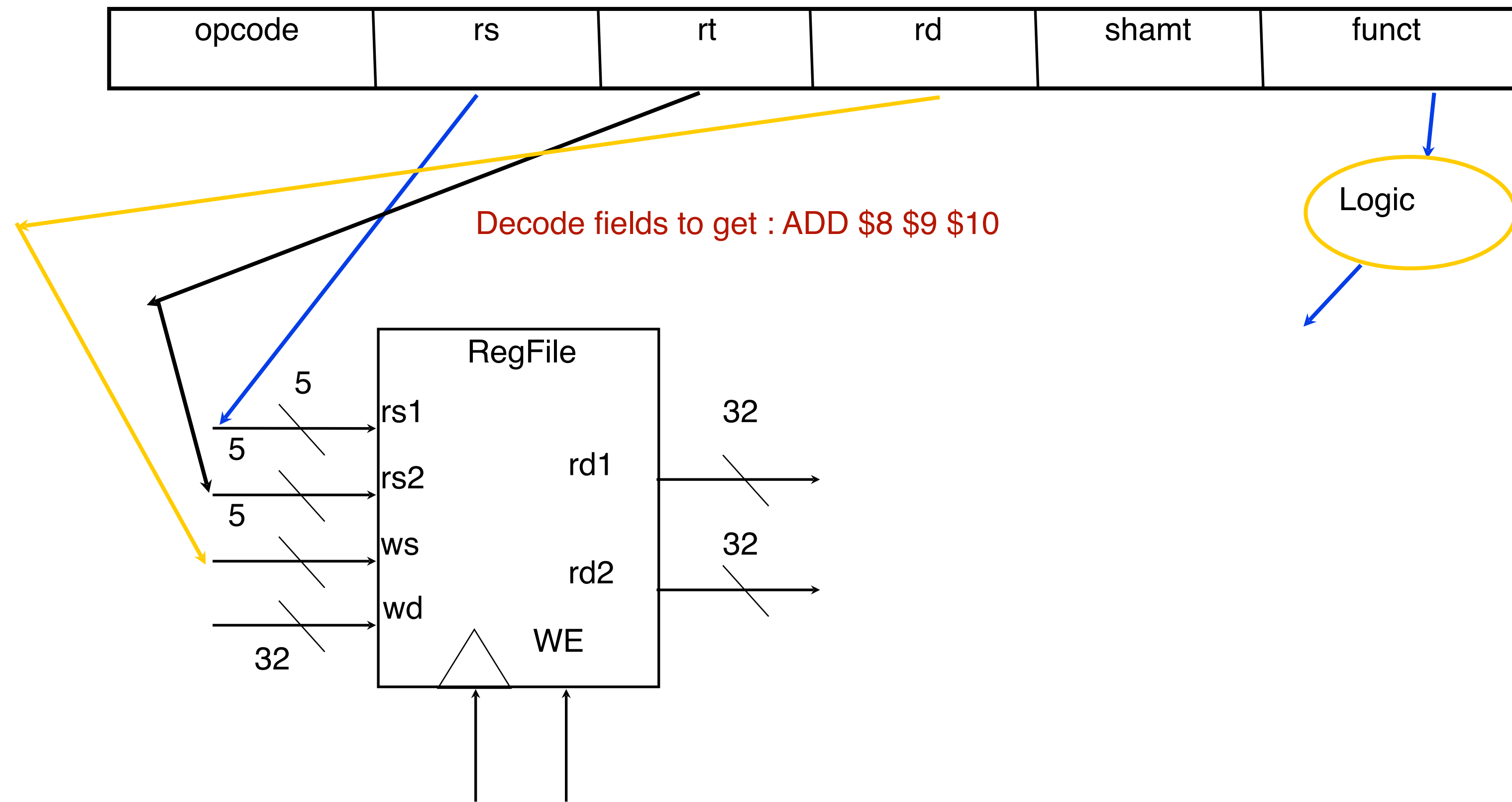

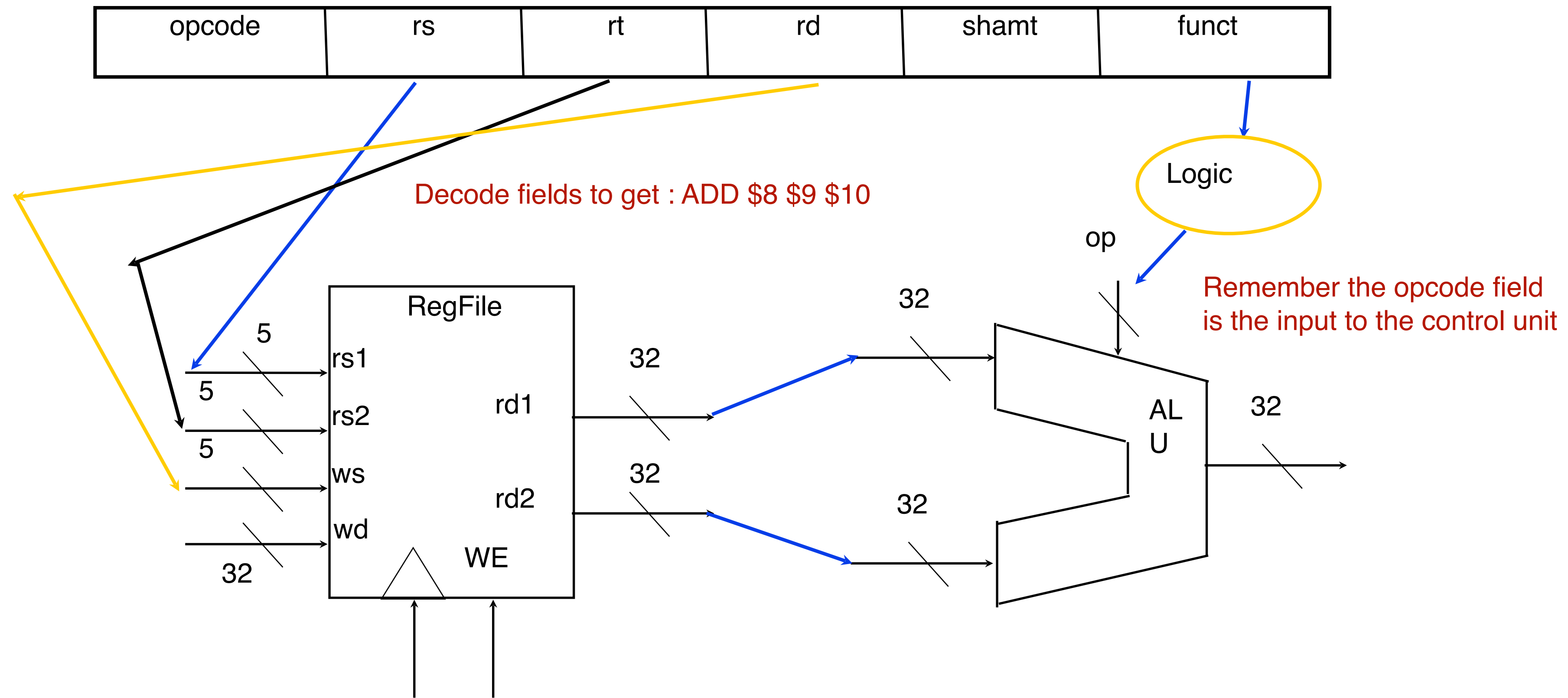
Datapath Elements: Executing Instructions



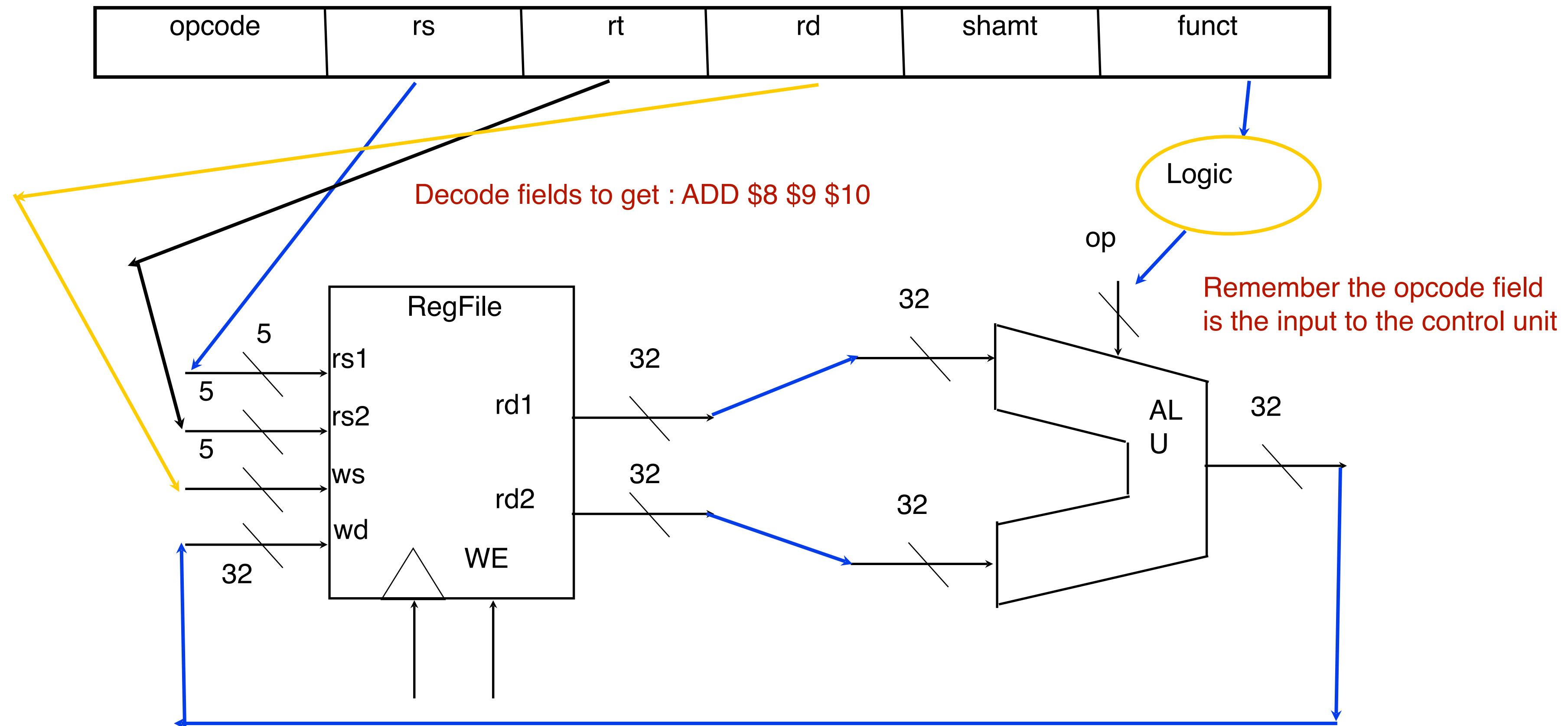
Datapath Elements: Executing Instructions




Datapath For Instruction Fetch

 



Datapath For Instruction Fetch

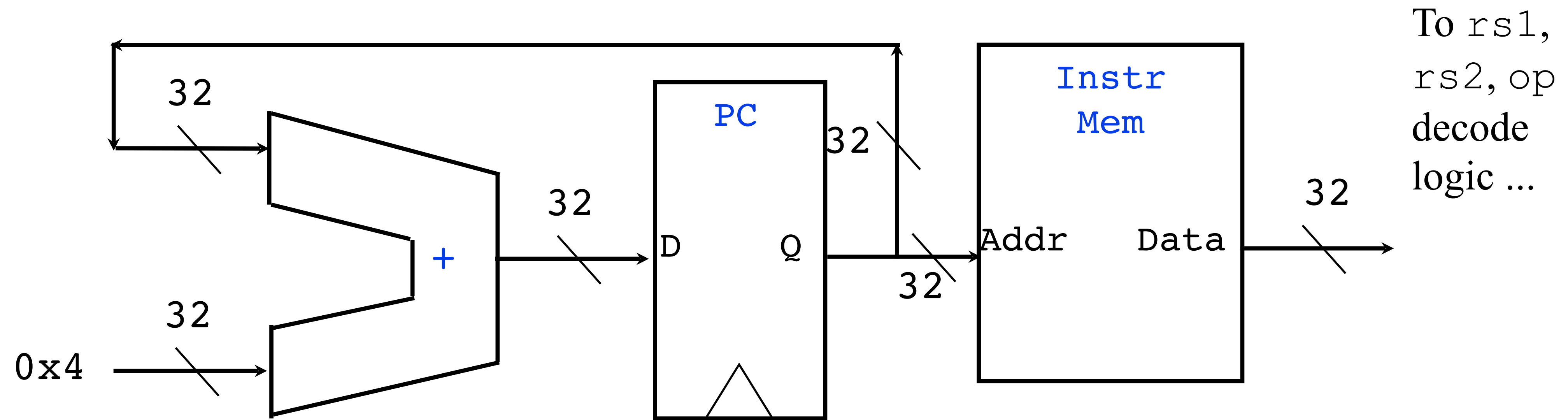

What about I format?

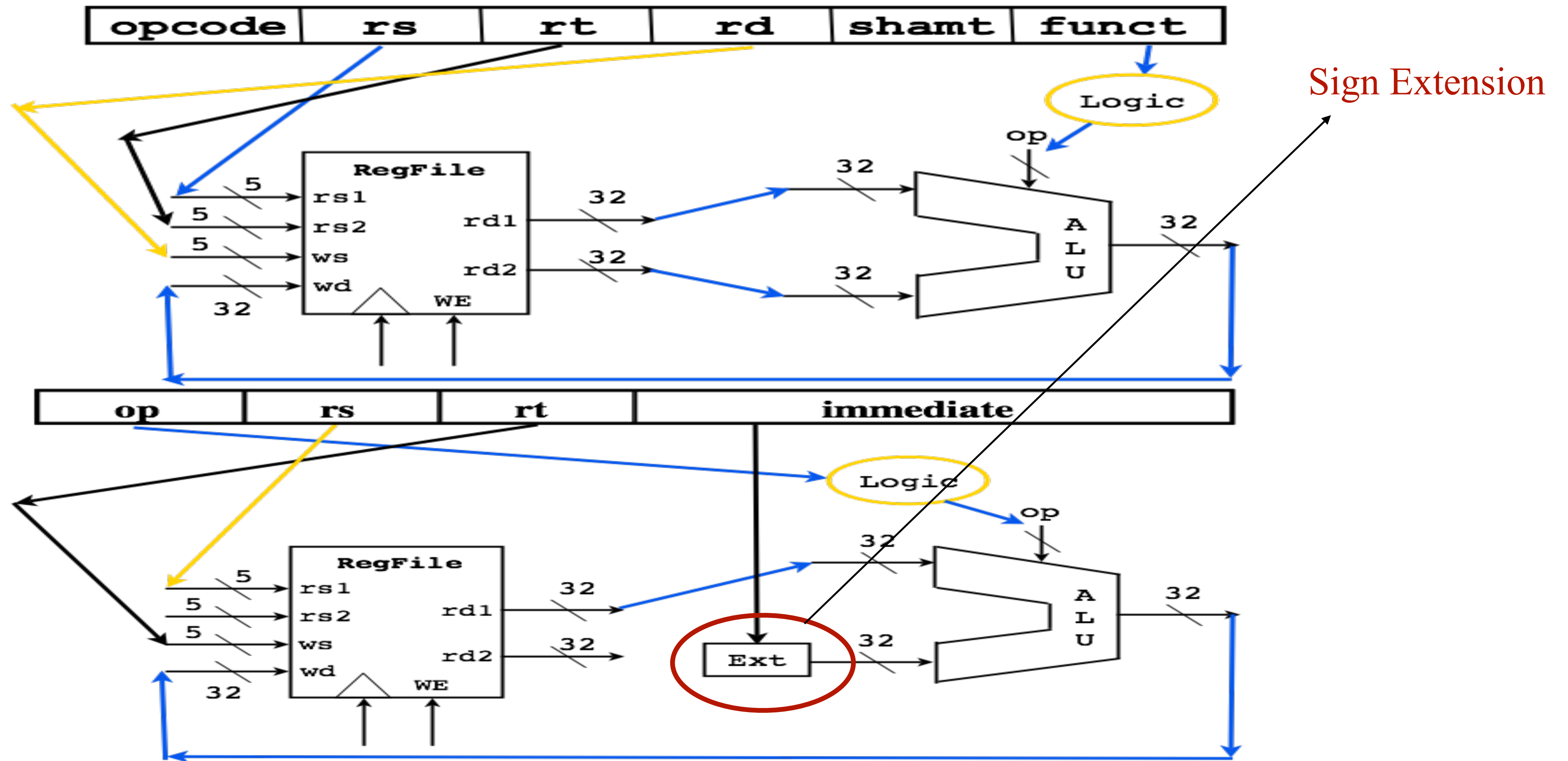


Loads from Memory

 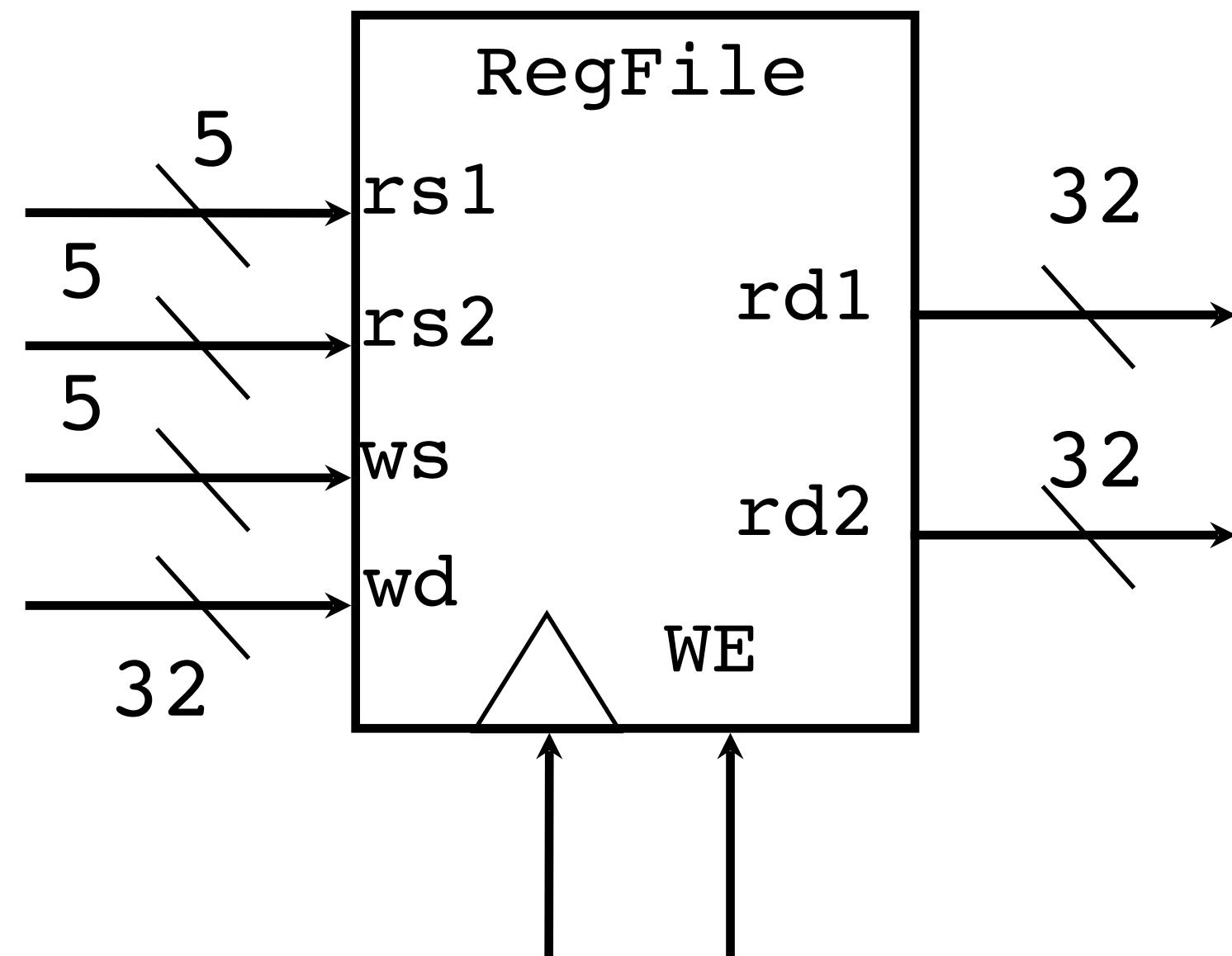

Syntax: `LW $1, 32($2)`

Action: $\$1 = M[\$2 + 32]$


Loads from Memory

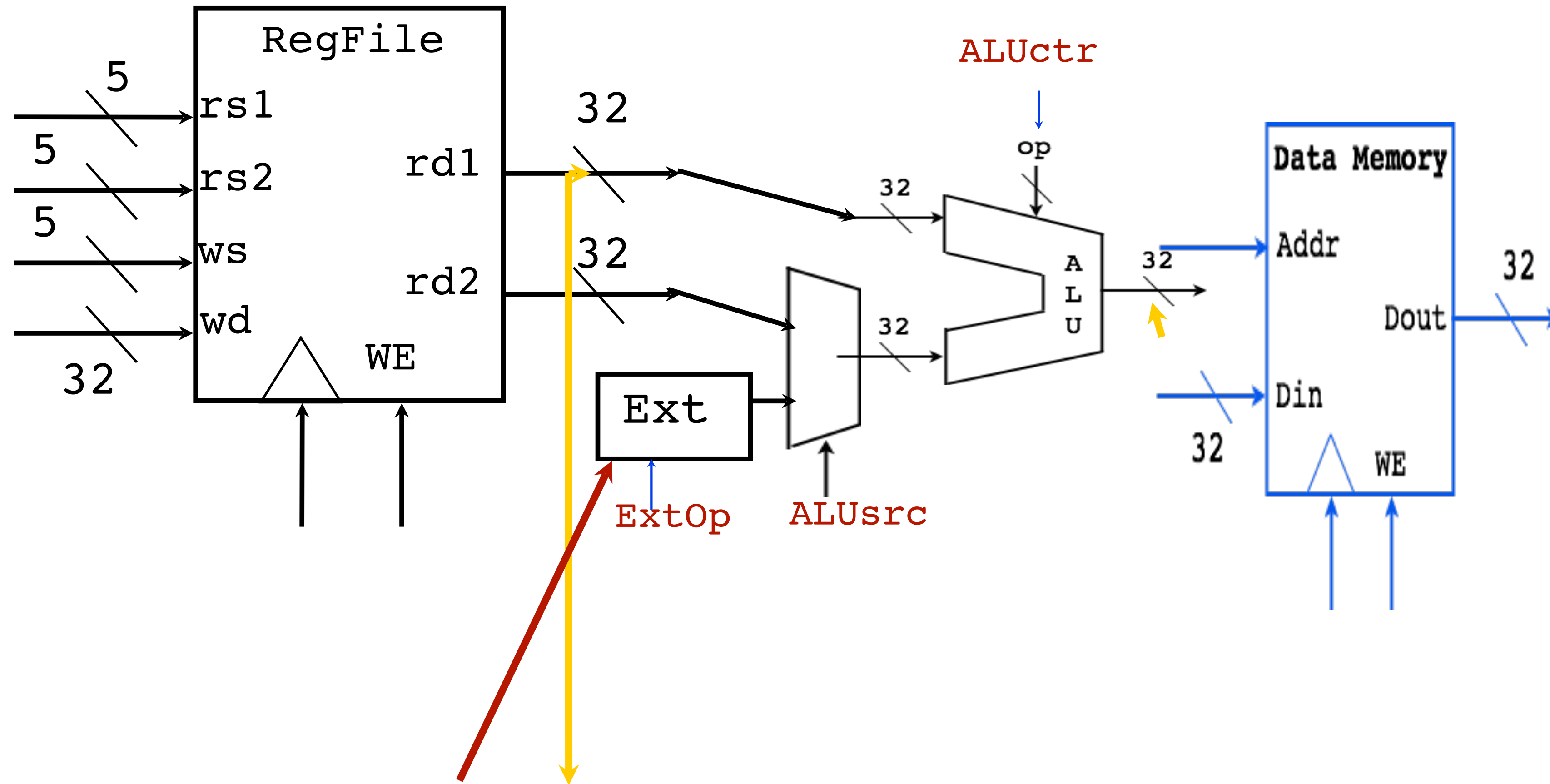

Syntax: `LW $1, 32($2)`

Action: $\$1 = M[\$2 + 32]$


Loads from Memory

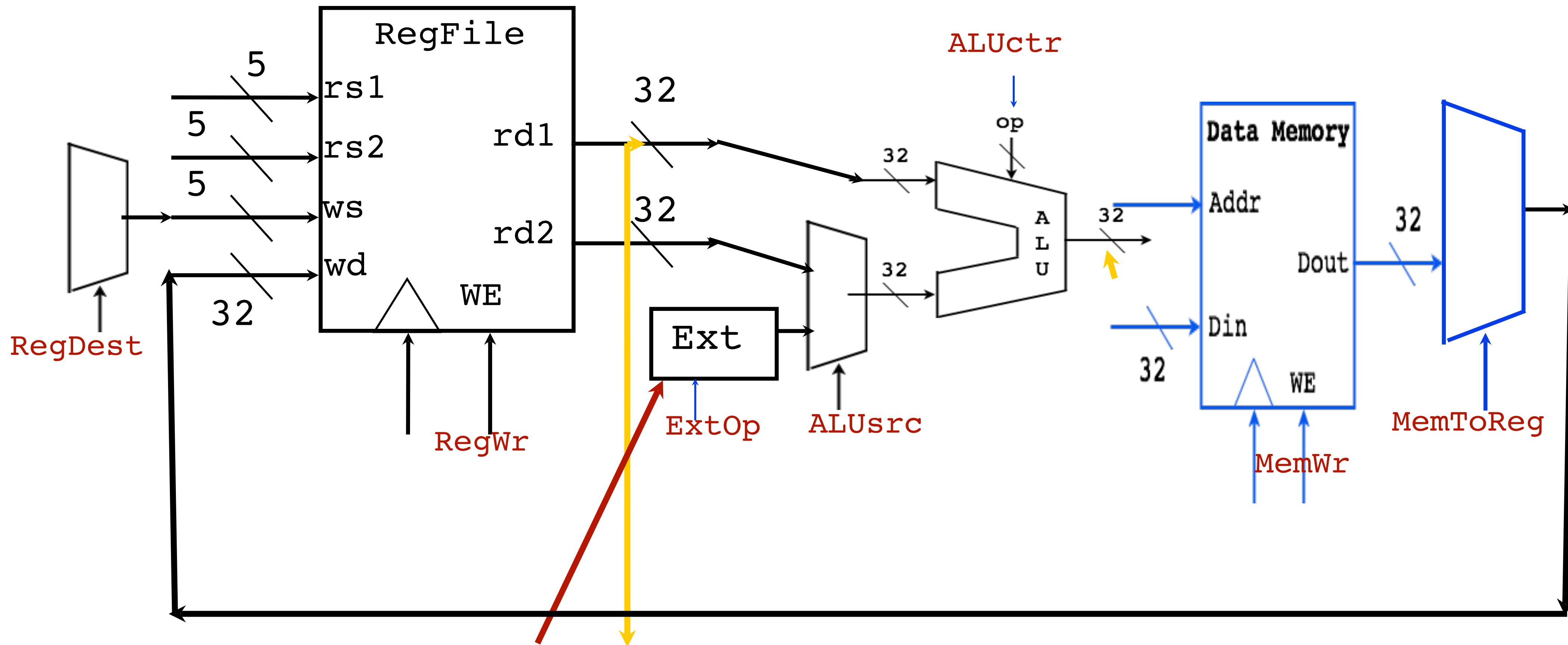

Syntax: `LW $1, 32($2)`

Action: $\$1 = M[\$2 + 32]$

Stores to Memory (with Load Datapath)

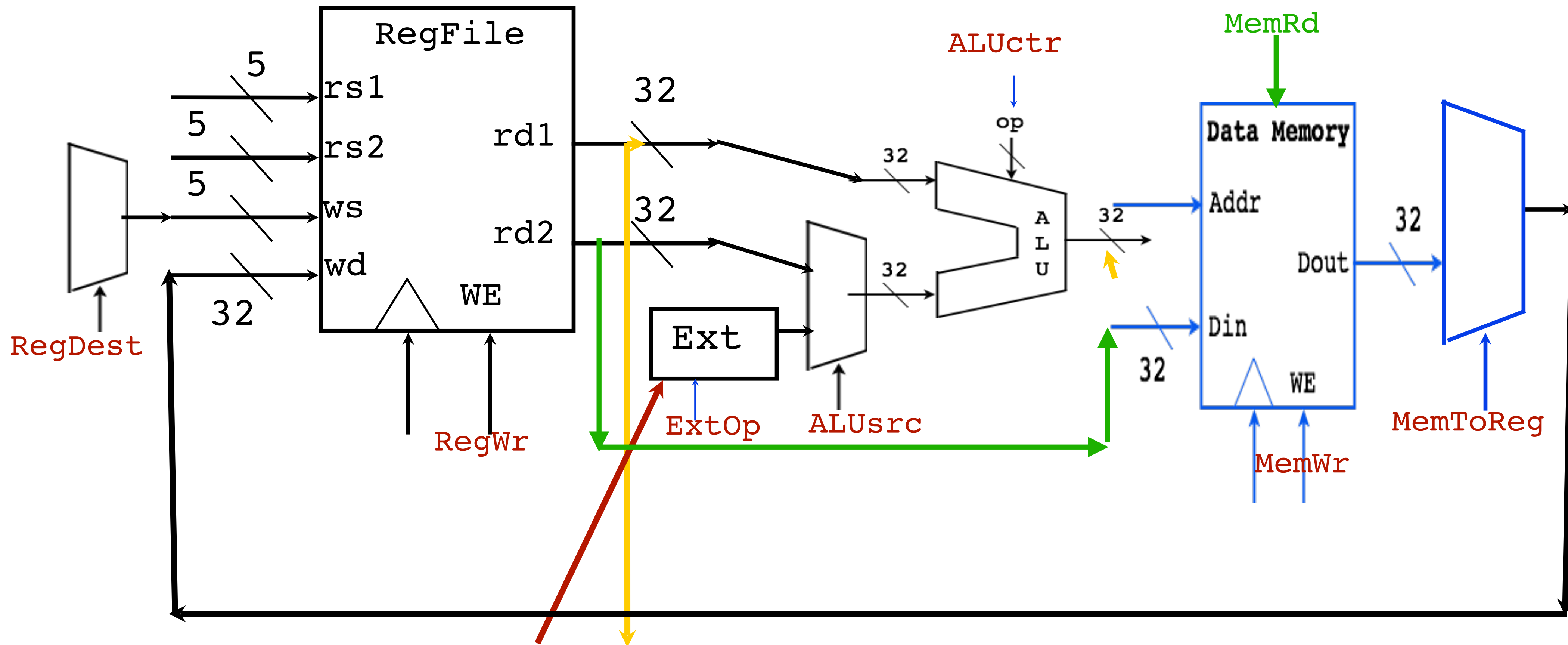

Syntax: SW \$1, 32(\$2)


Action: $M[\$2 + 32] = \1

Branch Instructions

Syntax: BEQ \$1, \$2, 12

Action: If $(\$1 \neq \$2)$, $PC = PC + 4$

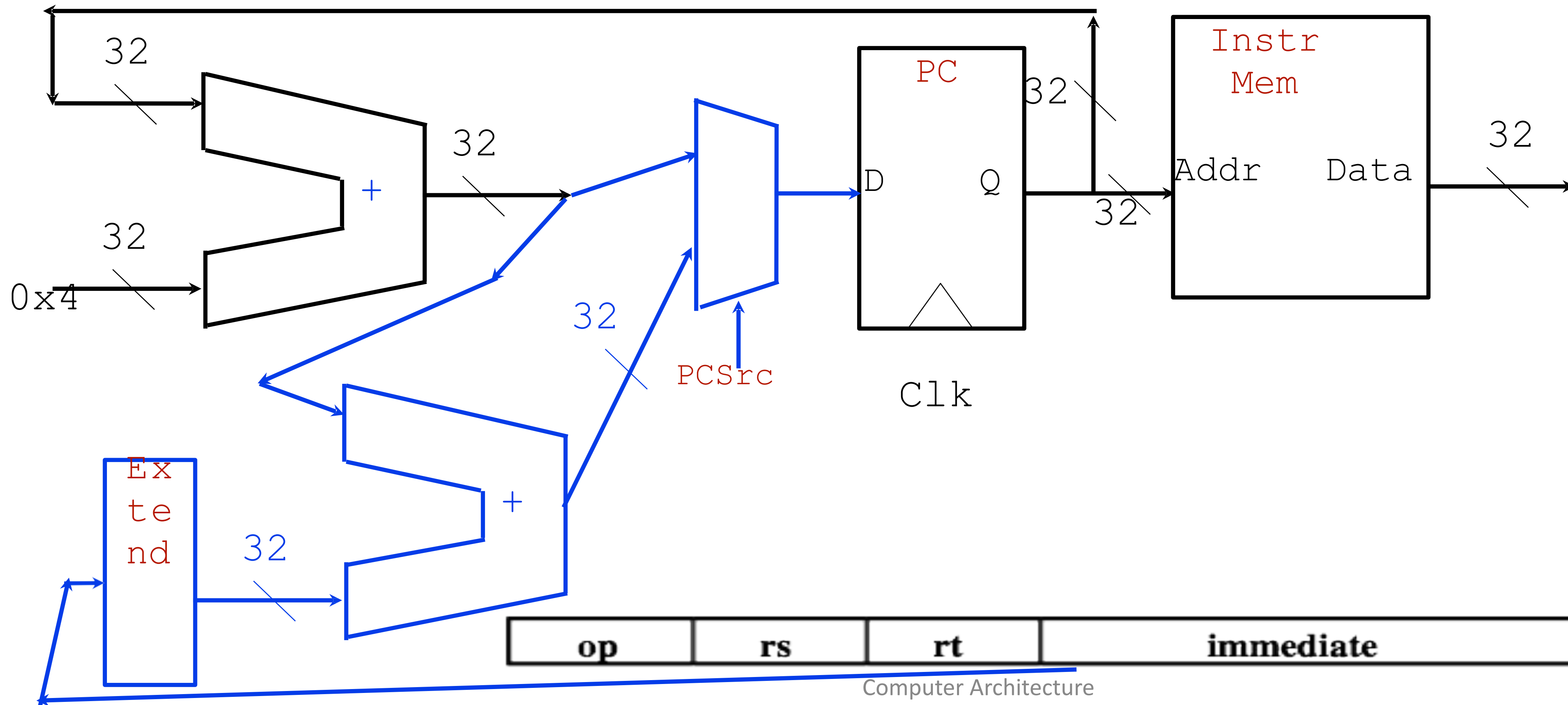Action: If $(\$1 == \$2)$, $PC = PC + 4 + 48$




Branch Instructions


Syntax: BEQ \$1, \$2, 12

Action: If (\$1 != \$2), PC = PC + 4

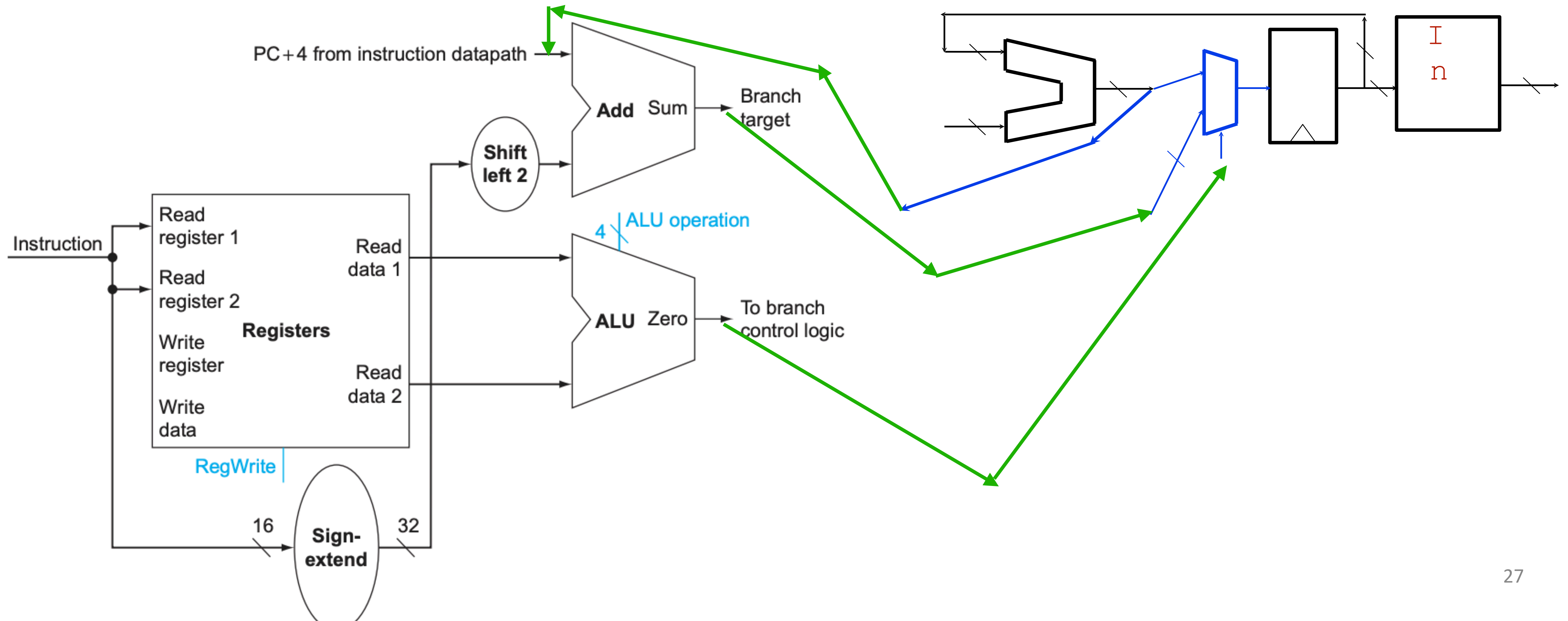Action: If (\$1 == \$2), PC = PC + 4 + 48




The Complete Picture

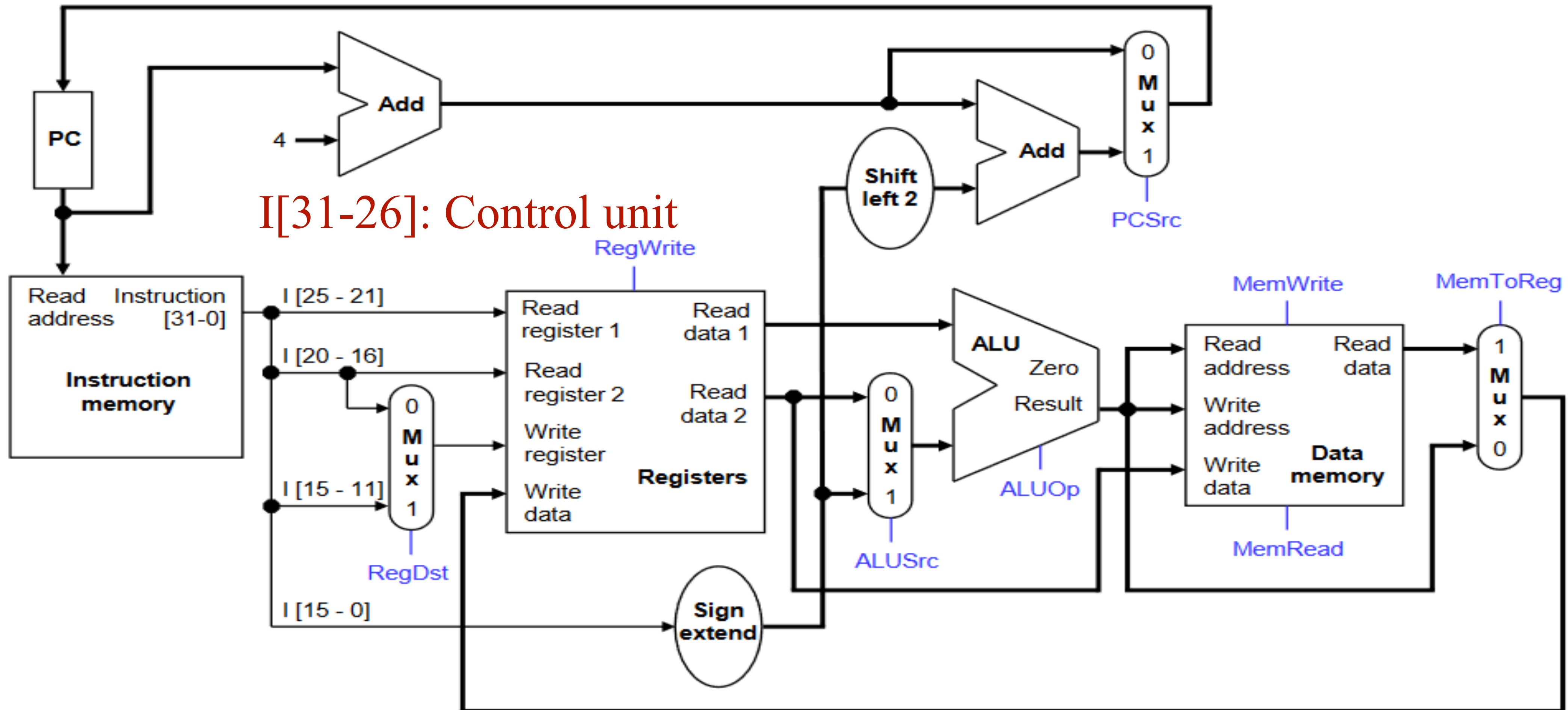

Control Signals So far

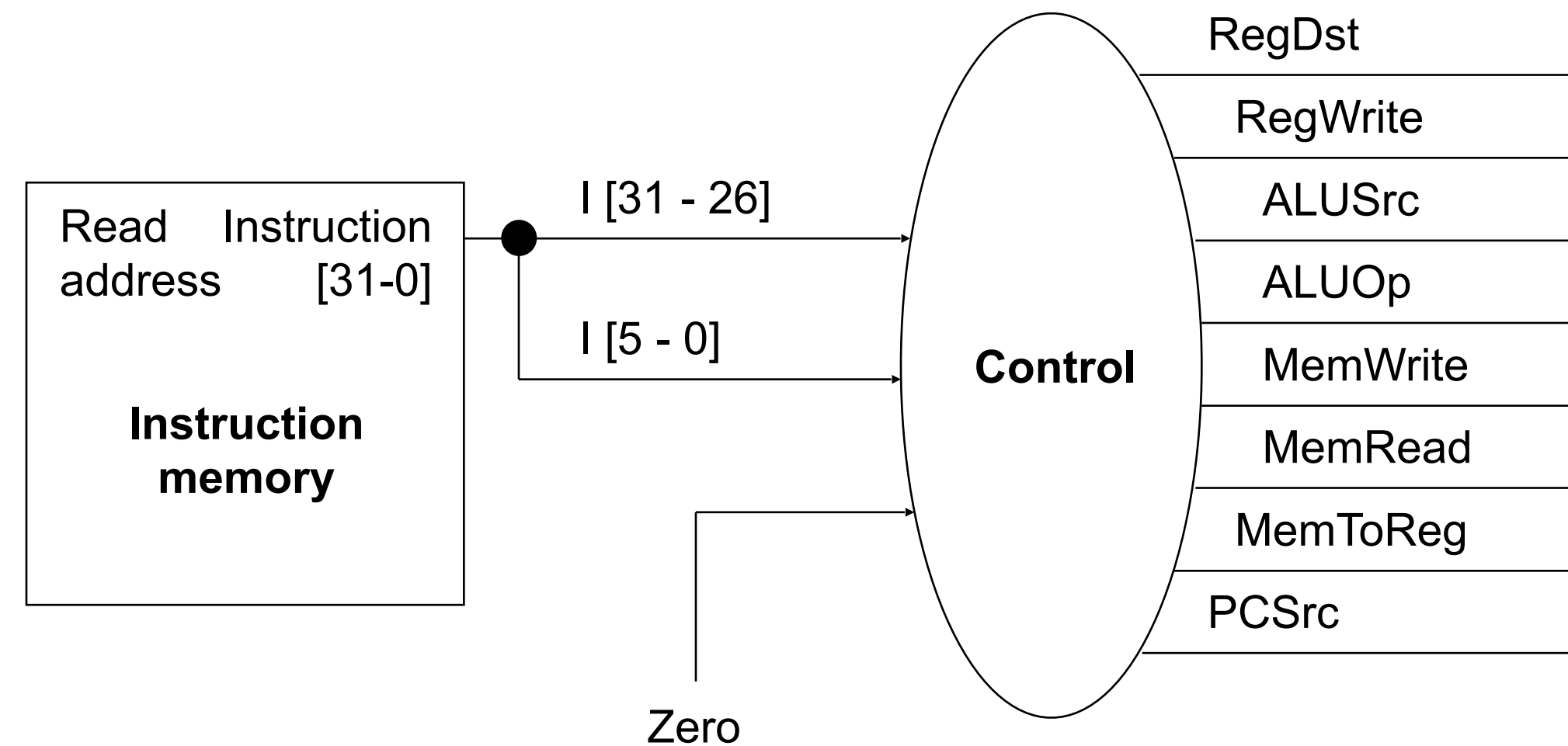- MemRead
- MemWrite
- RegWrite
- MemtoReg
- RegDst
- ALUOp, ALUSrc
- PCSrc



In Detail

- MemRead: Read from memory when **assert**
- MemWrite: Write into the memory when **assert**
- RegWrite: Reg. on **Write register** updated with the input, **on assert**
- MemtoReg: On **assert**, memory to register, on **deassert**, ALU to register
- RegDst: On **assert**, use rd field, on **deassert** use rt field
- ALUSrc: On assert, lower 16 bits of an inst., on **deassert** from the second register
- PCSrc: On assert, branch target, deassert, PC+4

Control Signal Table

| Operation | RegDst | RegWrite | ALUSrc | ALUOp | MemWrite | MemRead | MemToReg |
|-----------|--------|----------|--------|-------|----------|---------|----------|
| add | 1 | 1 | 0 | 010 | 0 | 0 | 0 |
| sub | 1 | 1 | 0 | 110 | 0 | 0 | 0 |
| and | 1 | 1 | 0 | 000 | 0 | 0 | 0 |
| or | 1 | 1 | 0 | 001 | 0 | 0 | 0 |
| slt | 1 | 1 | 0 | 111 | 0 | 0 | 0 |
| lw | 0 | 1 | 1 | 010 | 0 | 1 | 1 |
| sw | X | 0 | 1 | 010 | 1 | 0 | X |
| beq | X | 0 | 0 | 110 | 0 | 0 | X |

Why not single cycle?

- The longest possible datapath is the clock cycle time.

What does it mean?

Why not single cycle?


- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here.

| | | |
|---------------------------------|-----|-------|
| reading the instruction memory | 2ns | } 8ns |
| reading the base register \$sp | 1ns | |
| computing memory address \$sp-4 | 2ns | |
| reading the data memory | 2ns | |
| storing data back to \$t0 | 1ns | |

one clock cycle: 8ns

Processor frequency: 125MHz

Cycle per Instruction (CPI): 1

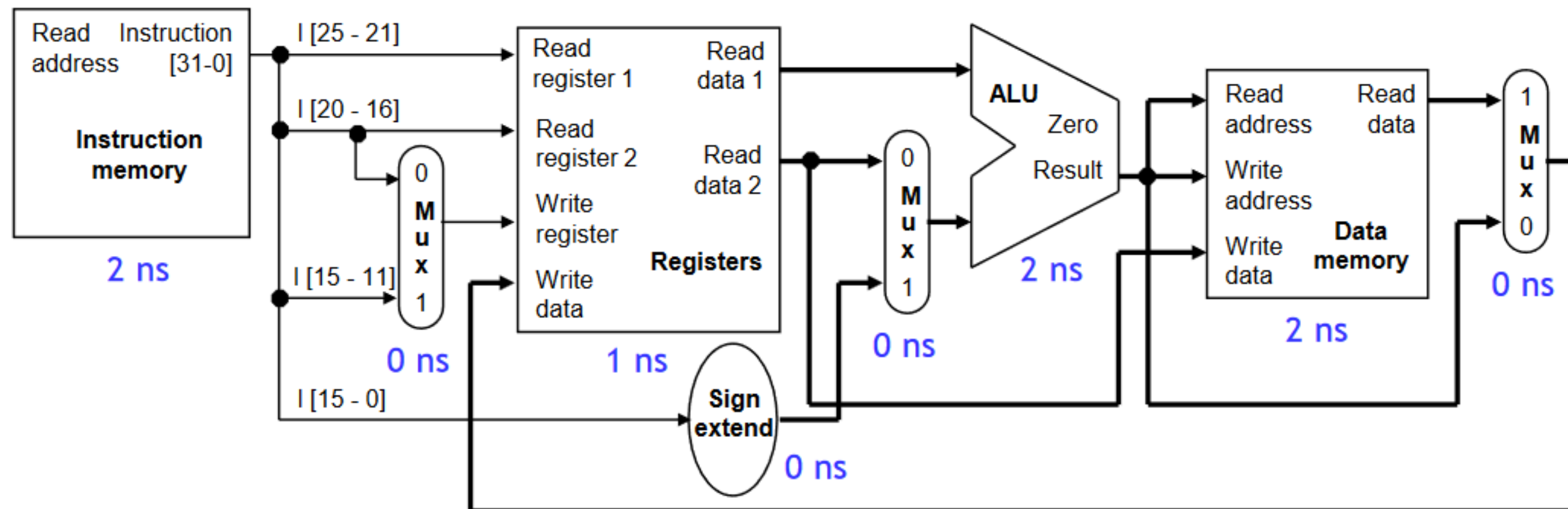

An add instruction:
no need of 8ns

Why not single cycle?


- The longest possible datapath is the clock cycle time.

Violating *common case fast* — Basic principle of computer architecture.

Now what should we do??

Why not single cycle?

A, B, C, D wants
to wash
cloths

 

Single Vs. Multi-cycle: Where is the Gain?

Single cycle (Worst case)

Everyone takes 90 mins Full package = 90 minutes

Multi cycle (average case kinda)

One person: 20 to 90 mins avg = 53.33 minutes

Single to Multi Cycle


- Measuring Performance:

$$Execution\ Time = \#Instructions \times Cycles\ Per\ Instruction \times Clock\ Cycle\ Time$$

$$Speedup = \frac{Execution\ Time_{old}}{Execution\ Time_{new}}$$

- Cycles Per Instruction (CPI) = 1 for single cycle processor
 - Very good, can't be better in simple scenarios
 - But still it's problematic — Why?
 - The clock cycle time is bounded by the length of the critical path of the datapath — here it is the load instruction
 - In simple words, the overall computation time will be poor!!!
- How can we improve?
 - Multi-cycle datapath: Improve clock frequency — but poor CPI — not a great option

Single to Multi Cycle

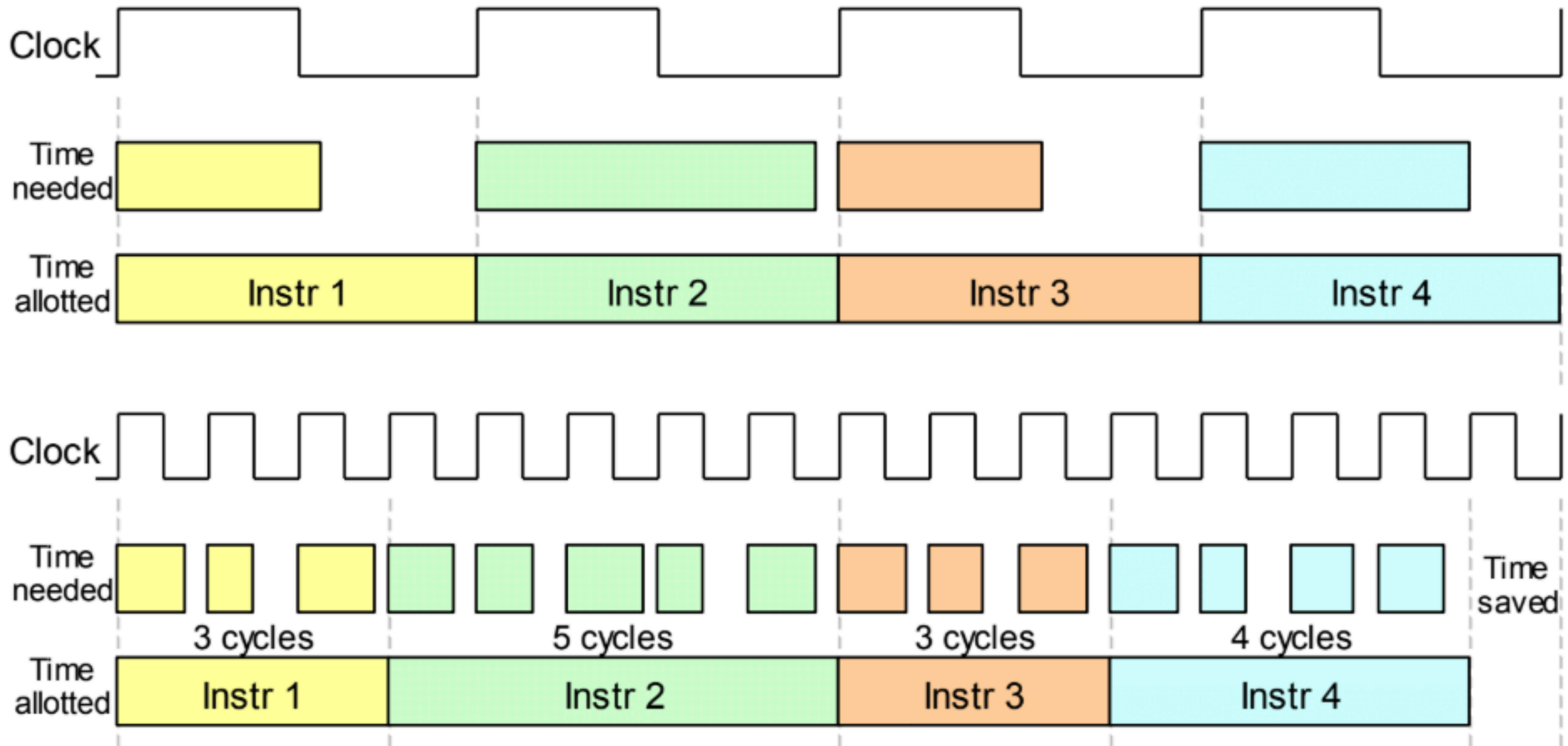





Can We Have Both?

Faster clock rate and also $CPI=1$?



Basic Intuition

A, B, C, D wants
to wash
cloths

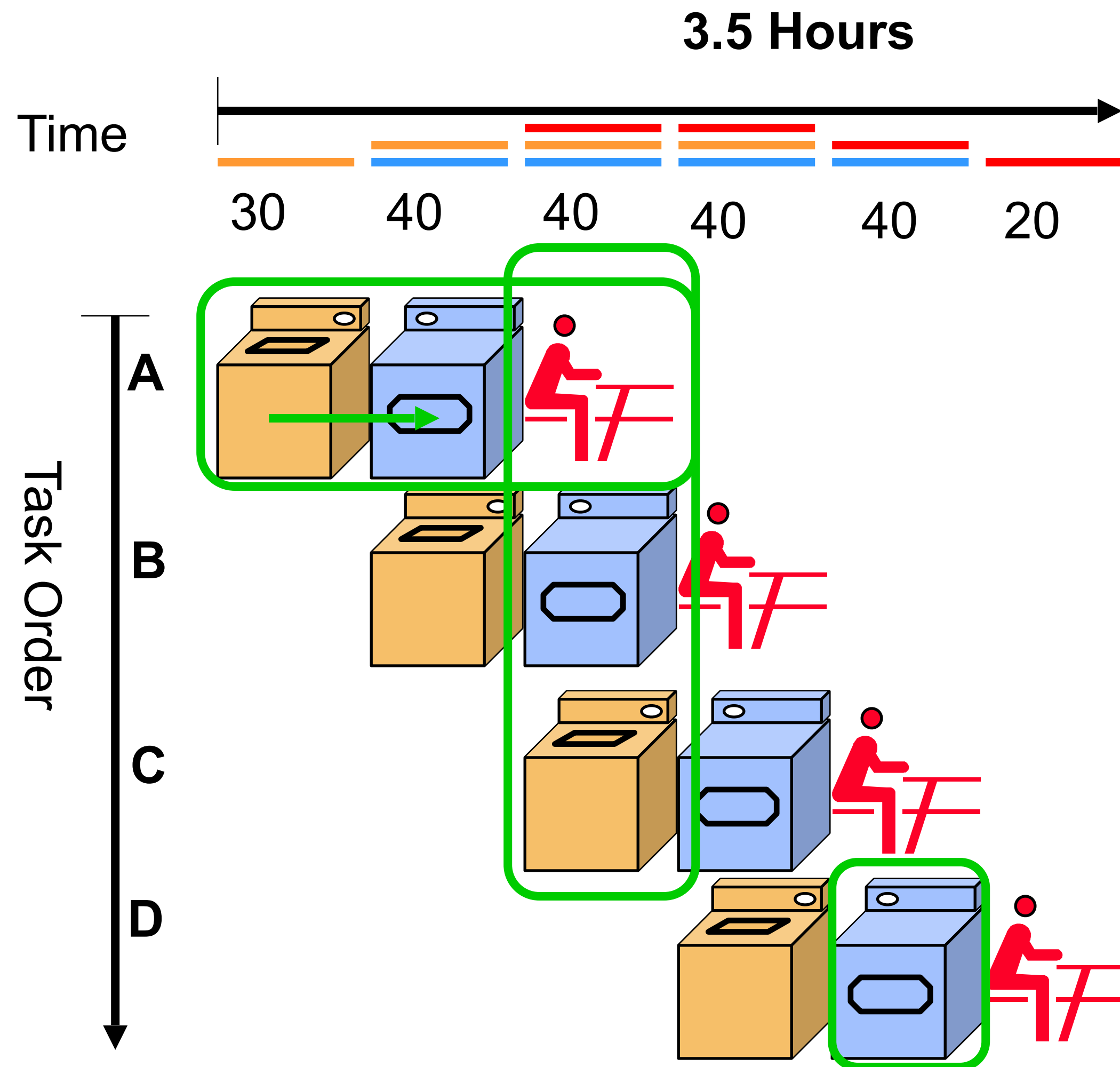   

Main Observations

- Different computation stages which can have overlapped tasks
 - This is the point of speedup!!!
- The timing of each computation stage is determined by the most time consuming task
- This is called **pipelining**
- **Tricky:**
 - Each person still needs 90 mins.
 - But considering all A, B, C, D, the average execution time improves a lot.

Latency and Bandwidth (throughput)

- Latency
 - time it takes to complete one instance
- Throughput
 - number of computations done per unit time

Following slides are adapted (with modifications) from Biswa's slides

Let's Summarize

Single cycle: CPI: 1 , Cycle time: long

Multi cycle: CPI: >1 , Cycle time: short


Pipelined: CPI: 1, Cycle time: short (improves throughput but not latency)

Pipelining and Richard Feynman

<https://www.youtube.com/watch?v=9miKIWIYi4w>

Jump to 1:25


Vanilla 5-stage pipeline

 


The right place to put the MUX that selects PC+4 and the target is the fetch stage.

The slide shows a vanilla 5-stage pipeline if we just take a single cycle datapath and divide it into five stages.


Resource Utilization

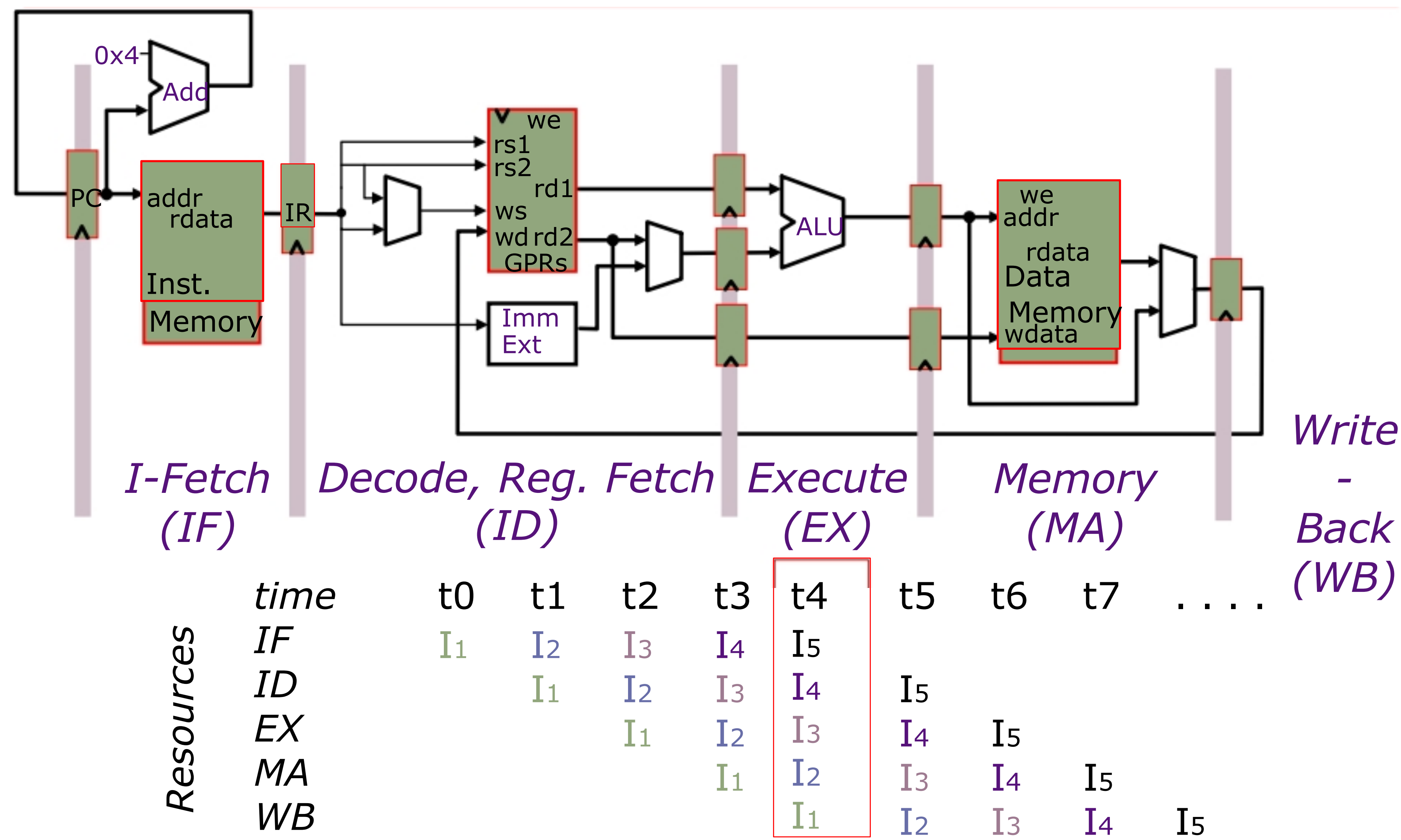

Visualizing Pipeline

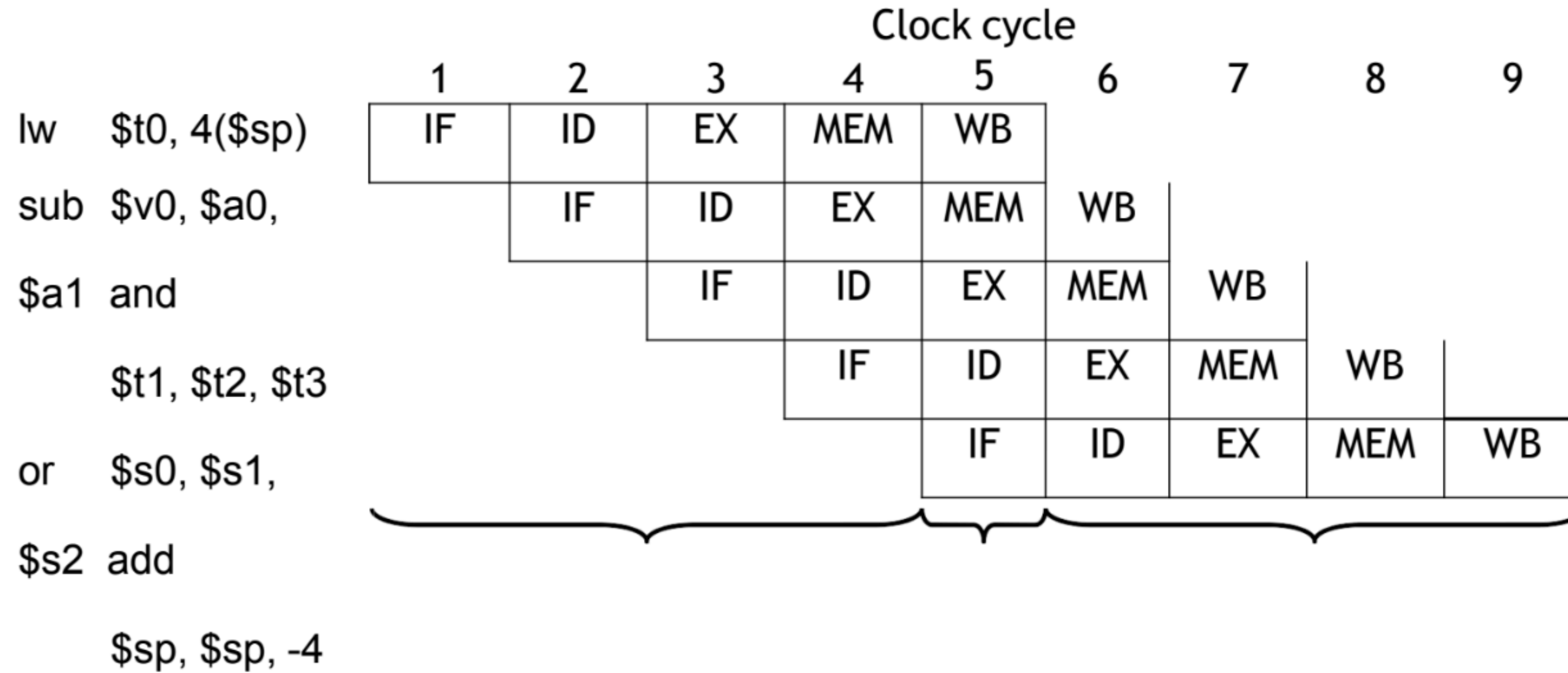

Visualizing Pipeline: Execution Time

 

For a k-stage pipeline executing N instructions

first instruction: K cycles

Next N-1 instructions: N-1 cycles, total = $K + (N-1)$ cycles

Pipelined versus Single cycle CPU design

| Instruction | Ifetch | Decode | Execute | Memory | Writeback | Total time |
|-------------|--------|--------|---------|--------|-----------|------------|
| LOAD | 200ns | 100 | 200 | 200 | 100 | 800ns |
| STORE | 200 | 100 | 200 | 200 | | 700ns |
| ADD | 200 | 100 | 200 | | 100 | 600ns |
| BRANCH | 200 | 100 | 200 | | | 500ns |

Total latency in single cycle CPU: **3200 ns**

Total latency in pipelined CPU (200ns clock cycle):

1000ns (1st instruction) + 3 X 200 ns (for next three) = 1600 ns

What's the big deal

$$\text{Speedup} = 3200\text{ns}/1600\text{ns} = 2X$$

What if we have a billion instructions?

$$\text{Single cycle} = 1 \text{ billion} * 800\text{ns} = 800 \text{ seconds}$$

$$\text{Pipelined} = 1000\text{ns} + (1 \text{ billion} - 1) * 200\text{ns} \sim 200 \text{ seconds}$$

$$\text{Speedup} = 4X \text{ ☺}$$

Let's include latch latency too

Inter-stage latch = 10ns

New clock cycle time in the pipelined design = 210ns

First instruction will get completed by 1040ns (five stages \times 200 ns + four inter-stage latches \times 10ns)

New Speedup = 800ns/210ns \sim 3.8X


How to Divide the Datapath?

Suppose memory is significantly slower than other stages. For example, suppose

| | |
|-----------|------------|
| t_{IM} | = 10 units |
| t_{DM} | = 10 units |
| t_{ALU} | = 5 units |
| t_{RF} | = 1 unit |
| t_{RW} | = 1 unit |

Since the slowest stage determines the clock, it may be possible to **combine some stages** without any loss of performance

Vanilla 5-stage pipeline

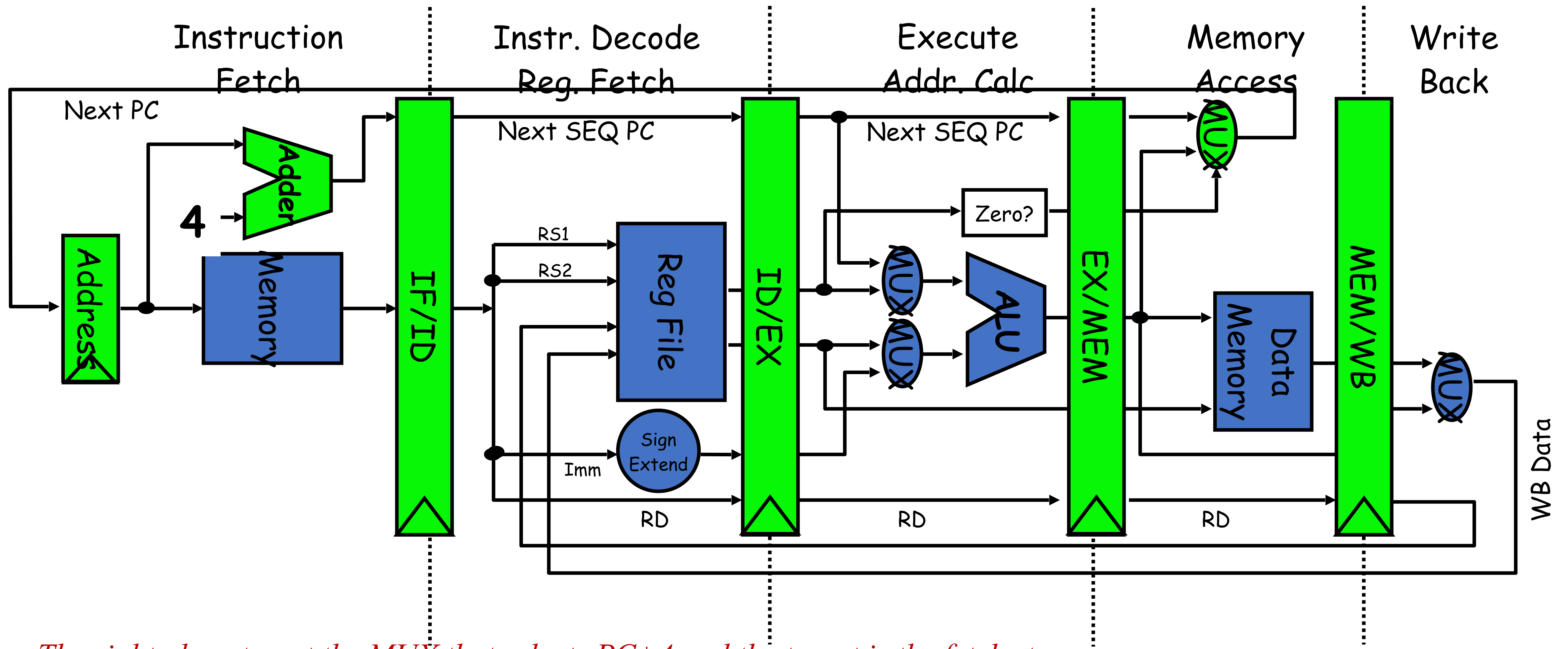


The right place to put the MUX that selects PC+4 and the target is the fetch stage.

The slide shows a vanilla 5-stage pipeline if we just take a single cycle datapath and divide it into five stages.


#Stages and Speedup

| Assumptions | Unpipelined t_c | Pipelined Speedup t_c | |
|---|----------------------|----------------------------|-----|
| 1. $t_{IM} = t_{DM} = 10$, $t_{ALU} = 5$, $t_{RF} = t_{RW} = 1$ 4-stage pipeline | 27 | 10 | 2.7 |
| 2. $t_{IM} = t_{DM} = t_{ALU} = t_{RF} = t_{RW} = 5$ 4-stage pipeline | 25 | 10 | 2.5 |
| 3. $t_{IM} = t_{DM} = t_{ALU} = t_{RF} = t_{RW} = 5$ 5-stage pipeline | 25 | 5 | 5.0 |


Stage-1: Fetch

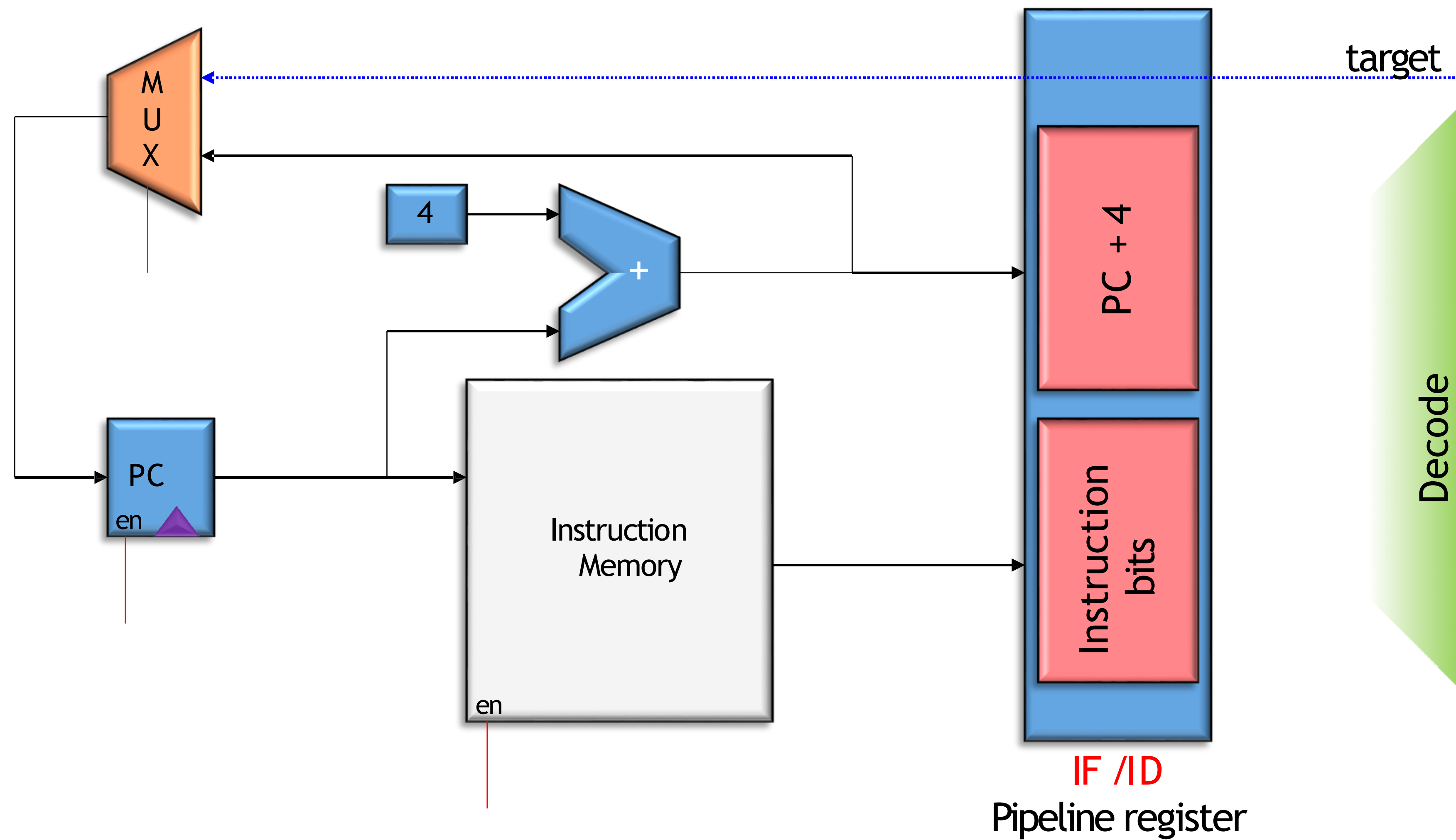


Stage 2: Decode

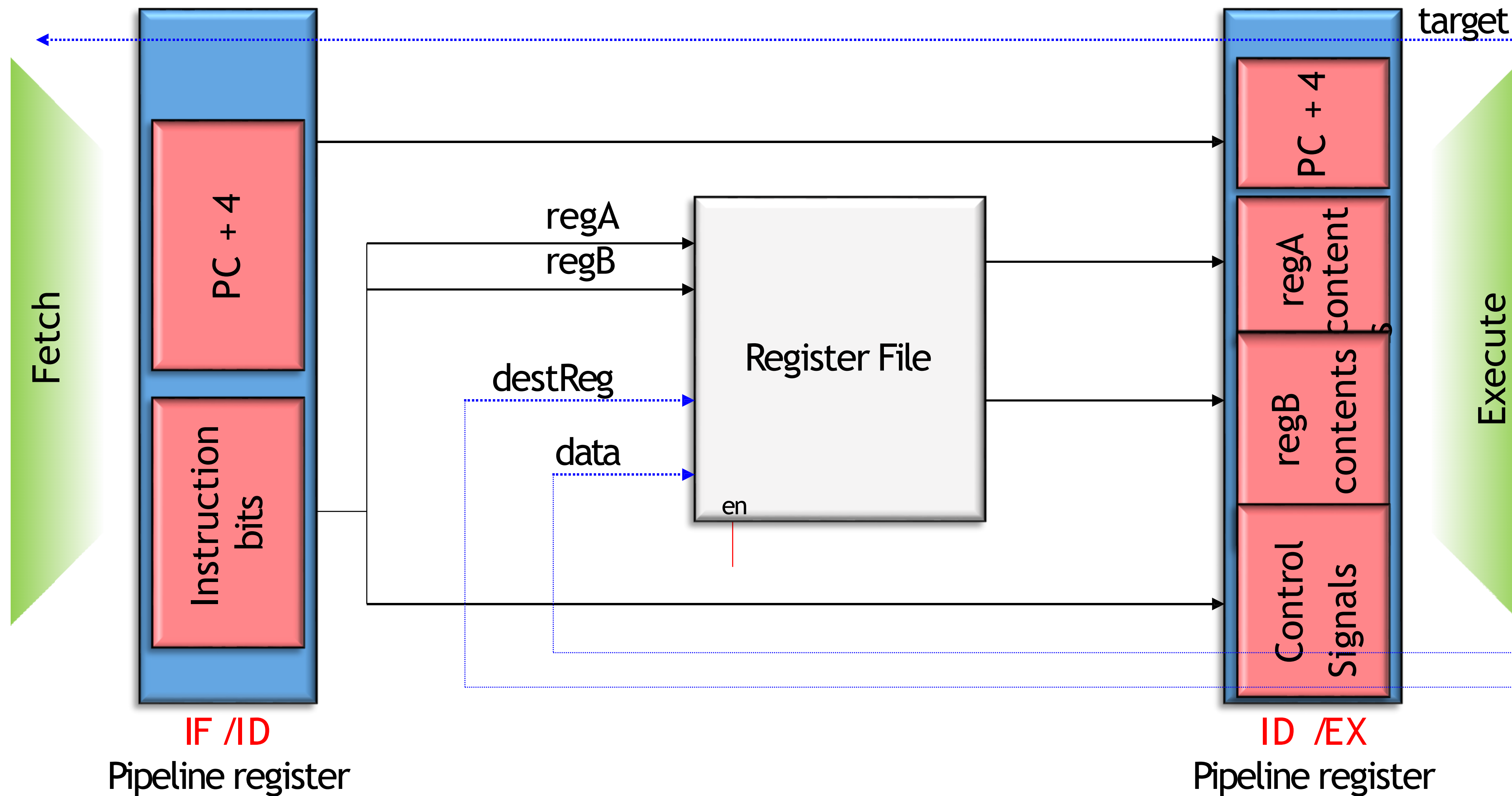


Stage 3: Execute

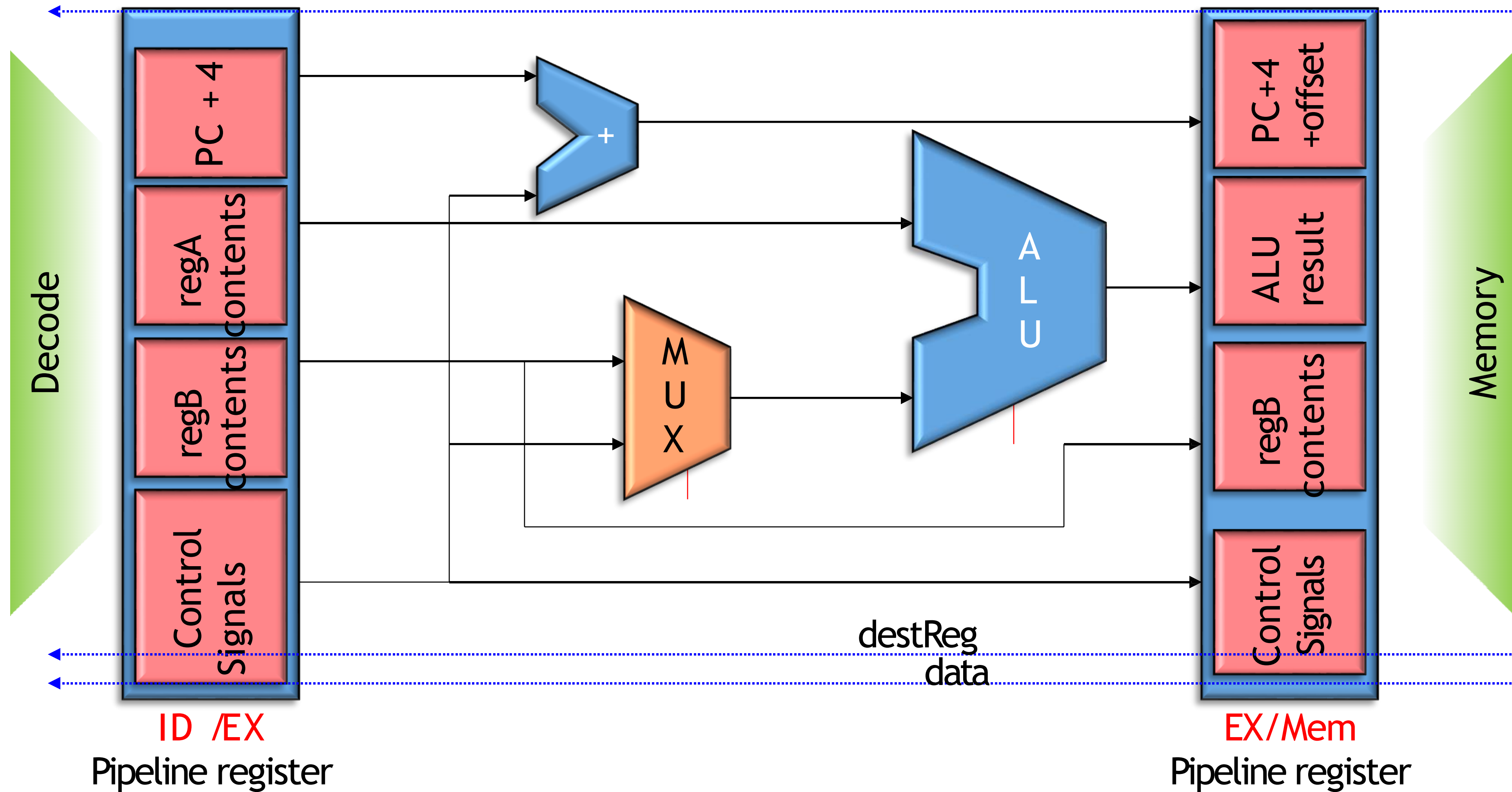

Stage 4: Memory Stage

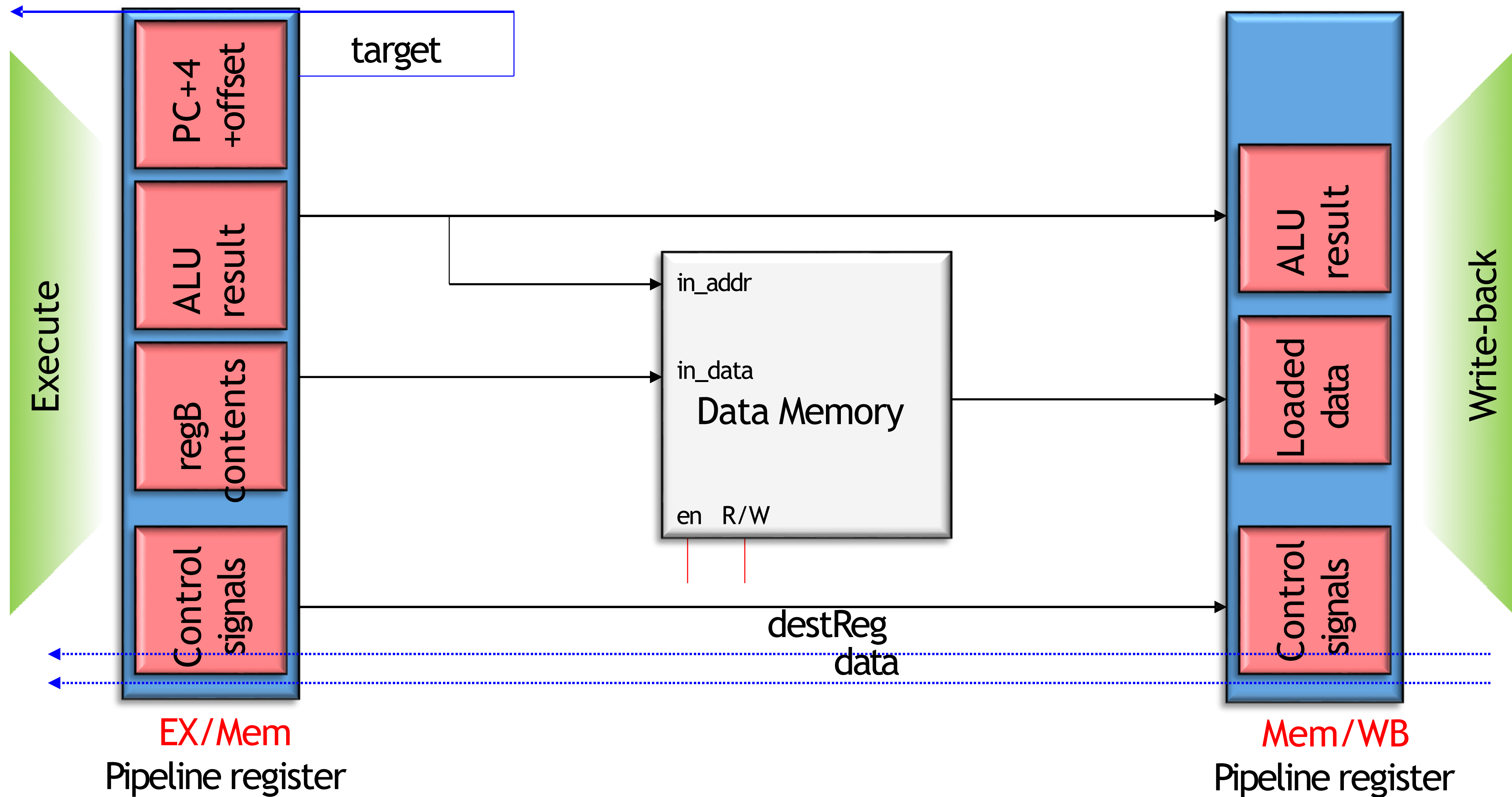

Stage 5: Write-back

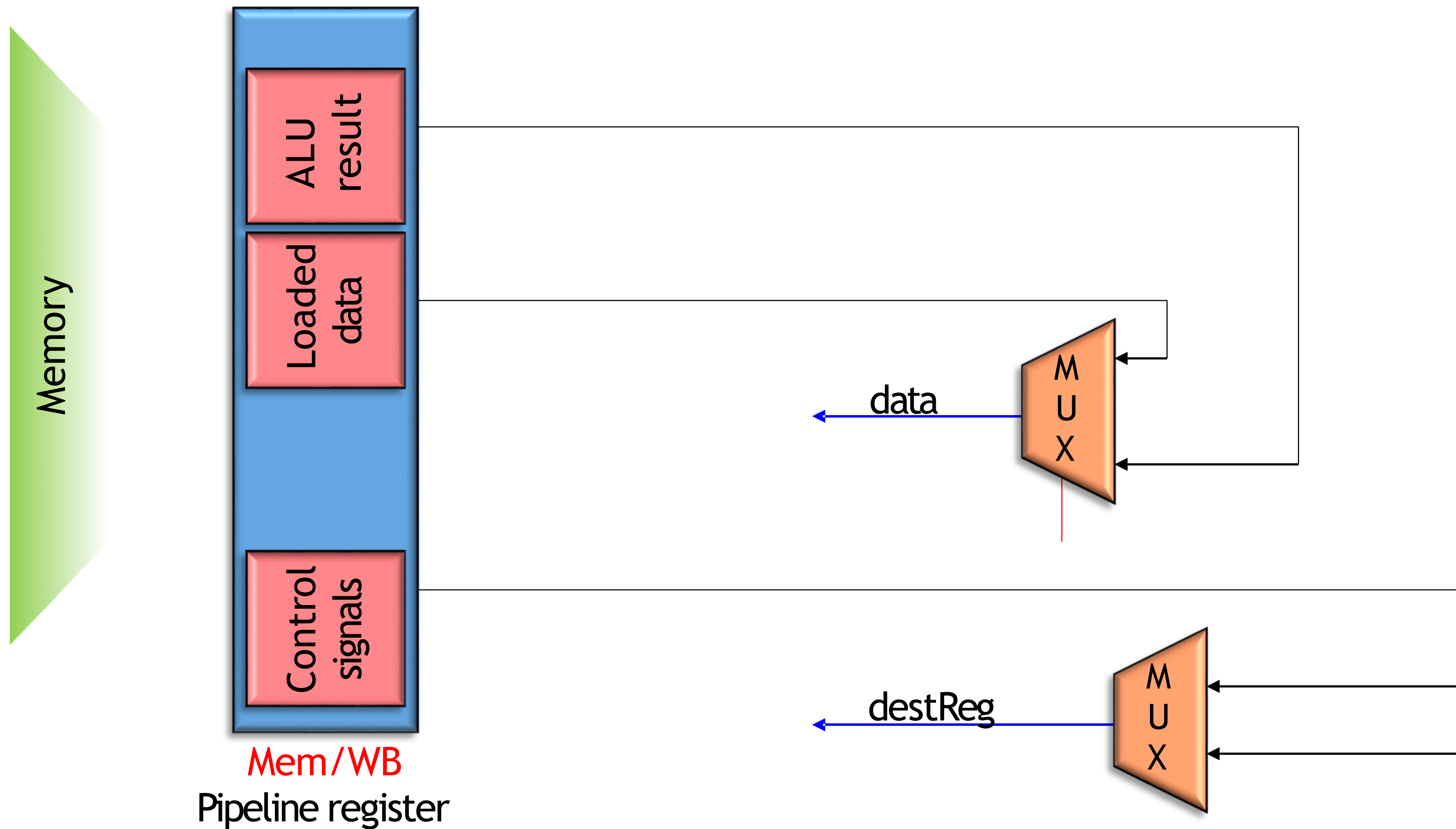

The Complete Picture

